

A Level • OCR • Physics

 16 mins  2 questions

Structured Questions

Capacitors in Circuits

Capacitance / Electron Flow in Charging & Discharging / Capacitors in Series & Parallel Circuits / Circuits Containing Capacitors & Resistors / Energy Stored by a Capacitor

Scan here to return to the course
or visit [savemyexams.com](https://www.savemyexams.com)




Total Marks

/16

- 1 (a)** The diagram below shows a circuit containing two capacitors which are both initially uncharged. The battery has e.m.f. E and negligible internal resistance.

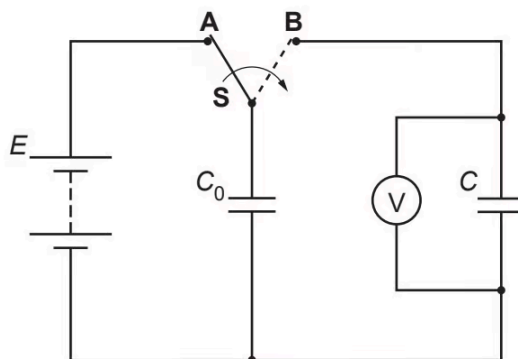The switch **S** is first moved to position **A** until the capacitor of capacitance C_0 is fully charged.



The switch **S** is then moved to position **B**. The initial charge stored by the capacitor of capacitance C_0 is shared between the two capacitors. The final reading on the voltmeter is V .

Show that $V = \frac{C_0}{C + C_0} E$.

[2]


(2 marks)

- (b)** A student wants to determine the values of E and C_0 by repeating the experiment above and measuring the potential difference (p.d.) V for a selection of capacitors of capacitance C .

The student decides to plot a graph of $\frac{1}{V}$ against C .

- i) Use the expression in **(a)** to show that the graph should be a straight line of gradient $\frac{1}{C_0 E}$ and y-intercept $\frac{1}{E}$.

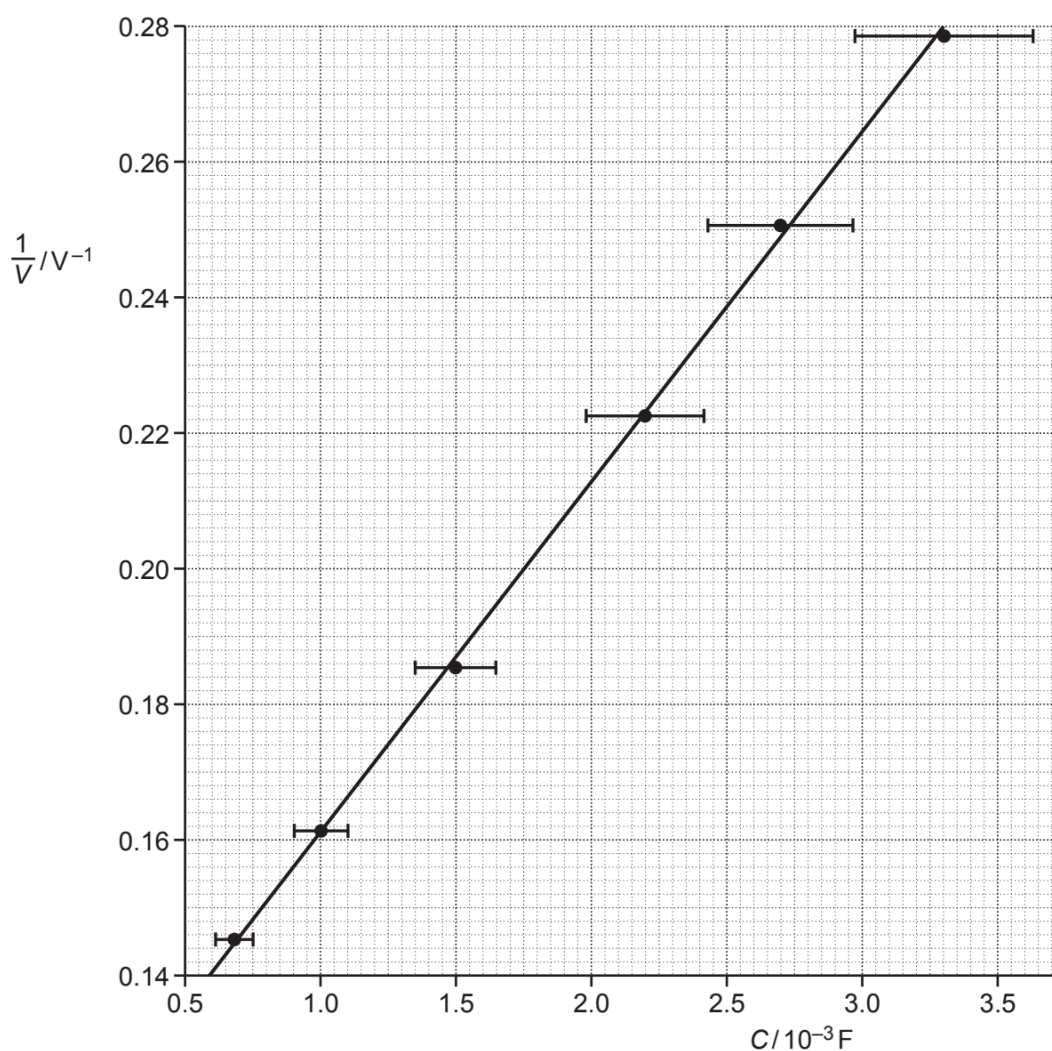ii) The data points, error bars and the line of best fit drawn by the student are shown in the graph below.



The gradient of the line of best fit is $51 \text{ V}^{-1} \text{ F}^{-1}$. The value of E is 9.1 V .

Determine the value of C_0 in millifarads (mF). Write your answer to 2 significant figures.

$C_0 = \dots\dots\dots \text{ mF}$ [2]

iii) Draw on the graph a straight line of worst fit.

Use this line to determine the absolute uncertainty in your value of C_0 . Write your answer to an appropriate number of significant figures.

absolute uncertainty = mF **[4]**

(7 marks)

- (c)** The experiment is repeated with a resistor of resistance $10\text{ k}\Omega$ placed in series between **S** and the capacitor of capacitance C_0 .

State with a reason what effect, if any, this would have on the experiment.

[1]

(1 mark)

- 2 (a)** A capacitor of capacitance 7.2 pF consists of two parallel metal plates separated by an insulator of thickness 1.2 mm . The area of overlap between the plates is $4.0 \times 10^{-4} \text{ m}^2$.

Calculate the permittivity of the insulator between the capacitor plates.

permittivity = F m^{-1} [2]

.....

..... (2 marks)

- (b)** Fig. 21 shows a circuit.

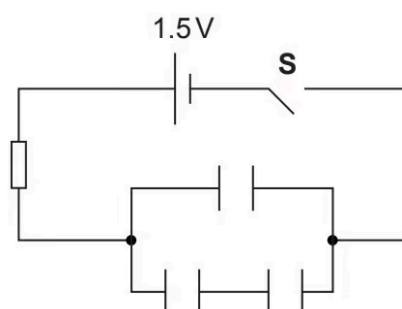


Fig. 21

The capacitance of each capacitor is $1000 \text{ }\mu\text{F}$. The resistance of the resistor is $10 \text{ k}\Omega$. The cell has e.m.f. 1.5 V and negligible internal resistance.

- i) Calculate the total capacitance C in the circuit.

$C = \dots\dots\dots \text{ }\mu\text{F}$ [2]

- ii) The switch **S** is closed at time $t = 0$. There is zero potential difference across the capacitors at $t = 0$.

Calculate the potential difference V across the resistor at time $t = 12 \text{ s}$.

$V = \dots\dots\dots \text{ V}$ [2]

.....

.....

(4 marks)