

A Level • OCR • Physics

 16 mins  2 questions

Structured Questions

Charging & Discharging Capacitors

Capacitor Charge & Discharge / Capacitor Charge & Discharge Equations /
Modelling Capacitor Discharge


Scan here to return to the course
or visit [savemyexams.com](https://www.savemyexams.com)



Total Marks

/16

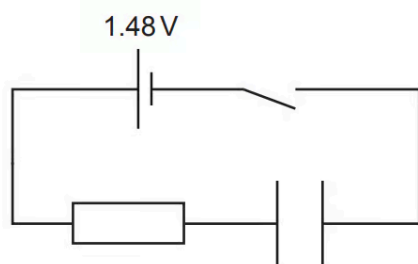1 (a) The diagram below shows a circuit to charge a capacitor.



The electromotive force (e.m.f.) E of the cell is 1.48 V and it has negligible internal resistance. The resistance of the resistor is 120 k Ω and the capacitance of the capacitor is 2000 μF . At time $t = 0$ the capacitor is uncharged. The switch is closed at time $t = 0$.

Calculate the time t when the potential difference across the capacitor is 1.00 V.

$t = \dots\dots\dots$ s [4]

.....


.....

.....

.....

(4 marks)

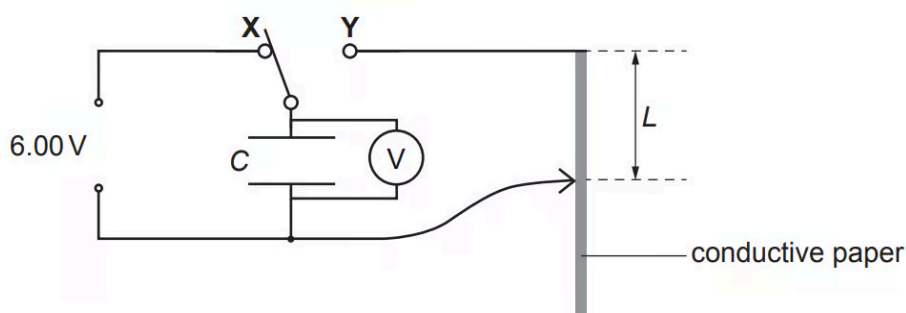(b) A capacitor of capacitance C is connected across a strip of conductive paper.



The switch is moved from X to Y, and the time t for the potential difference across the capacitor to halve is measured.

The time t is given by the expression


$$t = (Ck \ln 2) \times L$$

where k is the resistance of the conductive paper per unit length and L is the length of the conductive paper.

The value of C is $1.2 \times 10^{-3} \text{ F}$.

In an experiment, L is changed and t measured.

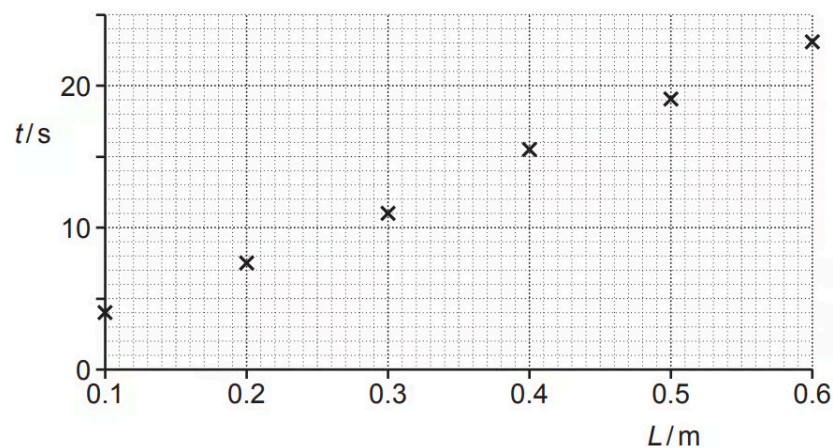The data points are plotted on a t against L grid as shown below.



Draw a straight line of best fit through the data points, and use the gradient of this line to determine k .

$$k = \dots\dots\dots \Omega \text{ m}^{-1} \text{ [4]}$$

(4 marks)

- 2 (a)** A student wishes to determine the permittivity ϵ of paper using a capacitor made in the laboratory. The capacitor consists of two large parallel aluminium plates separated by a very thin sheet of paper. The capacitor is initially charged to a potential difference V_0 using a battery. The capacitor is then discharged through a fixed resistor of resistance $1.0 \text{ M}\Omega$. The potential difference V across the capacitor after a time t is recorded by a data-logger. The student uses the data to draw the $\ln V$ against t graph shown in Fig. 22.

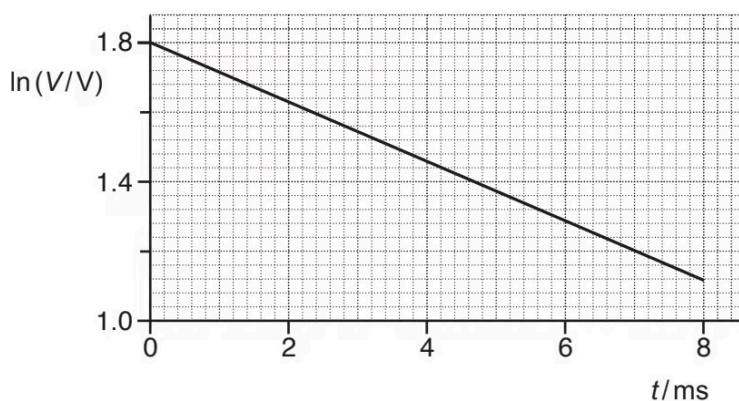


Fig. 22

Show that the magnitude of the gradient of the line shown in Fig. 22 is equal to

$$\frac{1}{CR}$$

where C is the capacitance of the capacitor and R is the resistance of the resistor.

[2]

(2 marks)

- (b)** Use Fig. 22 to determine the capacitance C of the capacitor. Describe how the student can then use this value of C to determine a value for ϵ . In your description, mention any additional measurements required on the capacitor.

[6]

.....

.....

.....

.....

.....

(6 marks)