


A Level • OCR • Physics

 7 mins 7 questions

Multiple Choice Questions

Charging & Discharging Capacitors

Capacitor Charge & Discharge / Capacitor Charge & Discharge Equations /
Modelling Capacitor Discharge


Medium (6 questions)	/6
Hard (1 question)	/1
Total Marks	/7

Scan here to return to the course
or visit [savemyexams.com](https://www.savemyexams.com)



Medium Questions

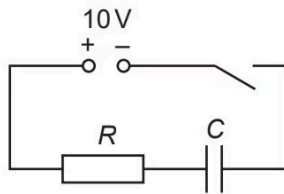- 1 The diagram below shows a circuit used to charge a capacitor.



The power supply has electromotive force (e.m.f.) 10 V and negligible internal resistance. The capacitor has capacitance C and the resistor has resistance R . The switch is closed at time $t = 0$. The table below shows potential difference V across the resistor at various values of time t .

V / V	10	6.3	5.0	3.7
t / s	0	2.8	4.2	6.0

What is the product $C \times R$ for this circuit?

- A. 0 s
- B. 2.8 s
- C. 4.2 s
- D. 6.0 s

(1 mark)

- 2 A capacitor discharges through a resistor. At time $t = 0$ the potential difference V across the capacitor is V_0 . At time $t = 2.0$ s, $V = 0.90 V_0$.

Which statement is **not** correct?

- A. At $t = 4.0$ s, $V = 0.81 V_0$.
- B. The capacitor is fully discharged after $t = 10$ s.
- C. The potential difference across the resistor is the same as that for the capacitor when the capacitor has potential difference $0.5V_0$.
- D. The potential difference V decreases exponentially with time t .

(1 mark)

- 3 A student is modelling the decay of charge for a capacitor discharging through a resistor using the equation $\frac{\Delta Q}{\Delta t} = -0.2Q$.

The student decides to use $\Delta t = 0.5$ s. The initial charge on the capacitor is $1000 \mu\text{C}$.

Part of the modelling spreadsheet from the student is shown below.

t / s	Charge Q left on capacitor at time t $/ \mu\text{C}$	Charge ΔQ decaying in the next 0.5 s $/ \mu\text{C}$
0	1000	100
0.5	900	
1.0		
1.5		

What is the value of Q in μC at $t = 1.5$ s?

- A. 700

- B. 720
- C. 729
- D. 800

(1 mark)


- 4 A capacitor discharges through a resistor. At time $t = 0$, the charge stored by the capacitor is $600 \mu\text{C}$. The capacitor loses 5.0% of its charge every second.

What is the charge **left** on the capacitor at time $t = 4.0 \text{ s}$?

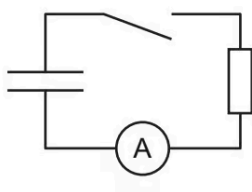- A. $111 \mu\text{C}$
- B. $120 \mu\text{C}$
- C. $480 \mu\text{C}$
- D. $489 \mu\text{C}$

(1 mark)

- 5 A capacitor is discharged through a resistor.




The capacitor is fully charged at time $t = 0$. The time constant of the circuit is 10 s . The switch is closed at time $t = 0$. The current in the resistor is I .

Which row is correct?

	Current I at $t = 0$	Current I at $t = 10 \text{ s}$
A	maximum	0
B	maximum	37% of the current at $t = 0$
C	0	63% of the current at $t = \infty$
D	0	37% of the current at $t = \infty$

(1 mark)

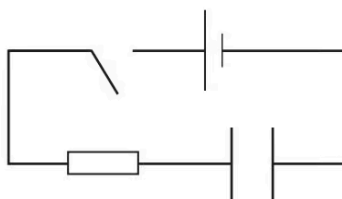6 A capacitor is charged through a resistor.




The cell has e.m.f. 1.50 V and negligible internal resistance. The capacitor is initially uncharged. The time constant of the circuit is 100 s. The switch is closed at time $t = 0$. What is the potential difference across the capacitor at time $t = 200 \text{ s}$?

- A.** 0.20 V
- B.** 0.55 V
- C.** 0.95 V
- D.** 1.30 V

(1 mark)

Hard Questions

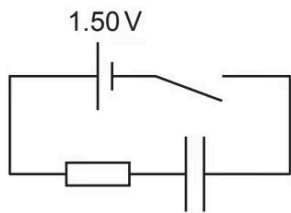- 1 A capacitor is charged through a resistor.



The cell has electromotive force (e.m.f.) 1.50 V and negligible internal resistance. The time constant of the circuit is 10 s. The switch is closed at time $t = 0$. At time t , the potential difference across the resistor is 0.60 V.

Which expression is correct?

- A. $0.60 = 1.50e^{-0.10t}$
- B. $0.90 = 1.50(e^{-10t} - 1)$
- C. $0.60 = 1.50e^{-10t}$
- D. $0.60 = 1.50(1 - e^{-0.10t})$

(1 mark)